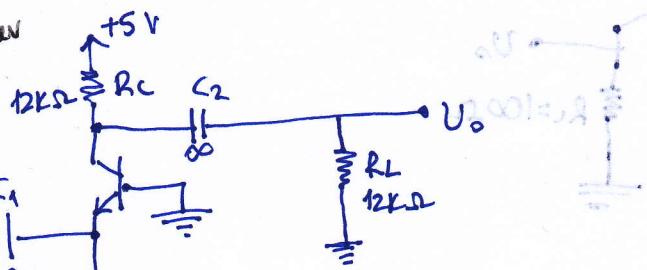
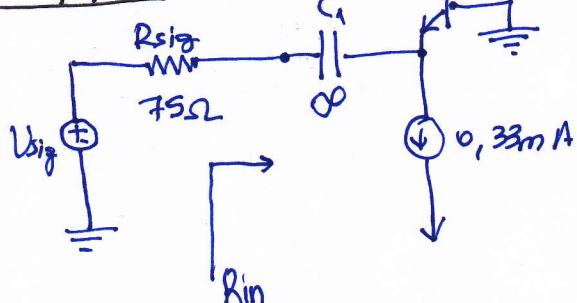
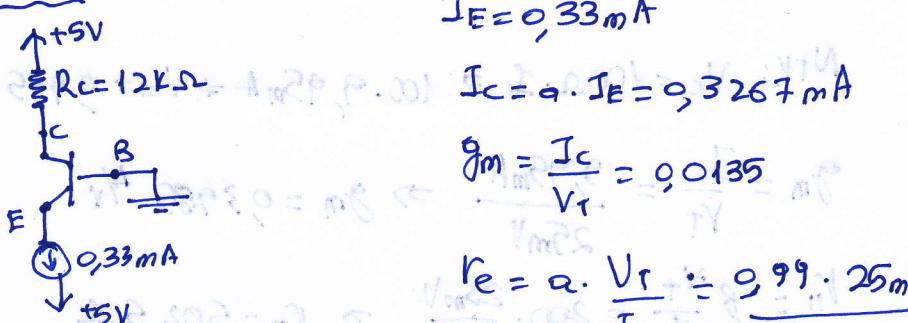
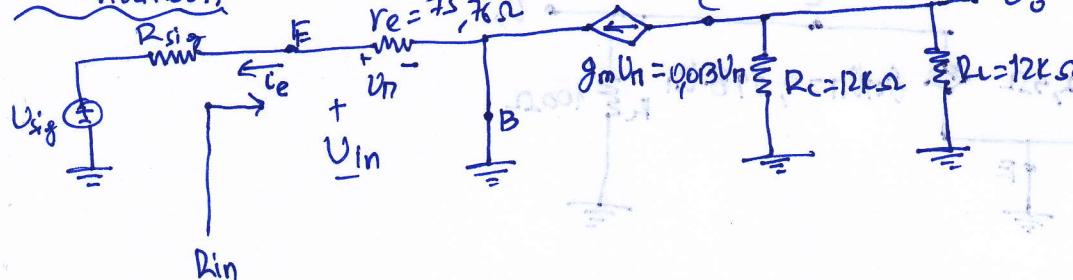


2<sup>η</sup> έργο ΑυτοτόνωνΆριθμος 1DC Ανάλυση:AC Ανάλυση:


$$\frac{U_o}{U_{sig}} = \frac{R_c / R_L \cdot i_c}{U_{sig}} = \frac{R_c / R_L \cdot g_m U_{in}}{U_{sig}} = \frac{R_c / R_L \cdot g_m r_e \cdot i_e}{U_{sig}} = \frac{R_c / R_L \cdot g_m r_e U_{sig}}{(R_{sig} + r_e) \cdot U_{sig}}$$

$$= \frac{R_c / R_L \cdot I_c \cdot \alpha \cdot V_t}{V_t \cdot I_c \cdot (R_{sig} + r_e)} = \alpha \frac{R_c / R_L}{R_{sig} + r_e} = 0.99 \frac{12k / 12k}{75\Omega + 75.76\Omega} = \frac{0.99 \cdot 6000}{150.76} = 39.4$$


$$R_{in} = \frac{U_{in}}{-i_e} = \frac{+r_e}{+i_e} \Rightarrow R_{in} = r_e = 75.76 \Omega$$

$$A_{v2} = -g_m \cdot R_L = -0.0135 \cdot 12k = -162$$

## Aufgabe 2

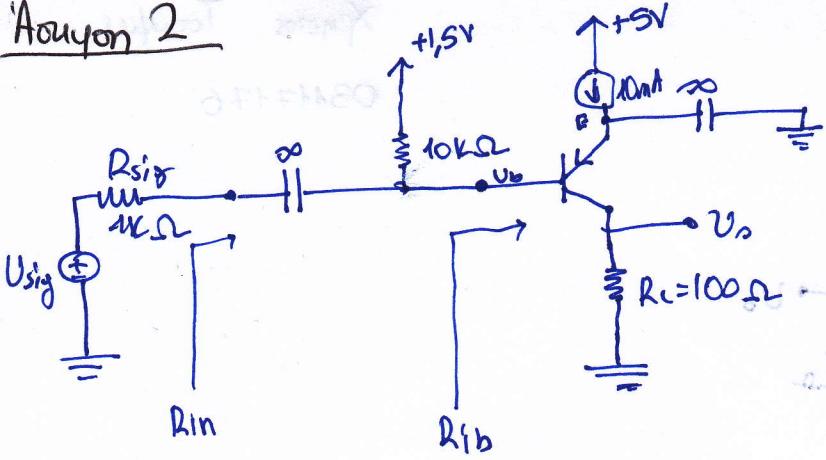

### DC Analysis:

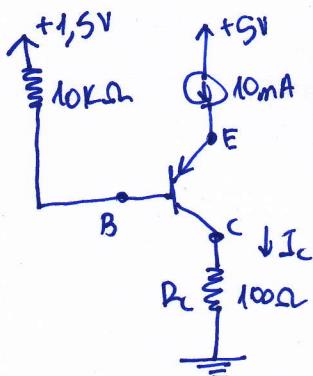

$$I_E = 10mA$$


$$I_C = \frac{\beta}{\beta+1} I_E = \frac{200}{201} \cdot 10mA \Rightarrow I_C = 9,95mA$$

$$\text{NTK: } V_C = 100\Omega \cdot I_C = 100 \cdot 9,95mA \Rightarrow V_C = -9,95V$$

$$g_m = \frac{I_C}{V_T} = \frac{9,95mA}{25mV} \Rightarrow g_m = 398,5 A/V$$

$$r_D = \frac{V_T}{\beta \frac{V_T}{I_C}} = 200 \cdot \frac{25mV}{9,95mA} \Rightarrow r_D = 502,5 \Omega$$

### AC Analysis:

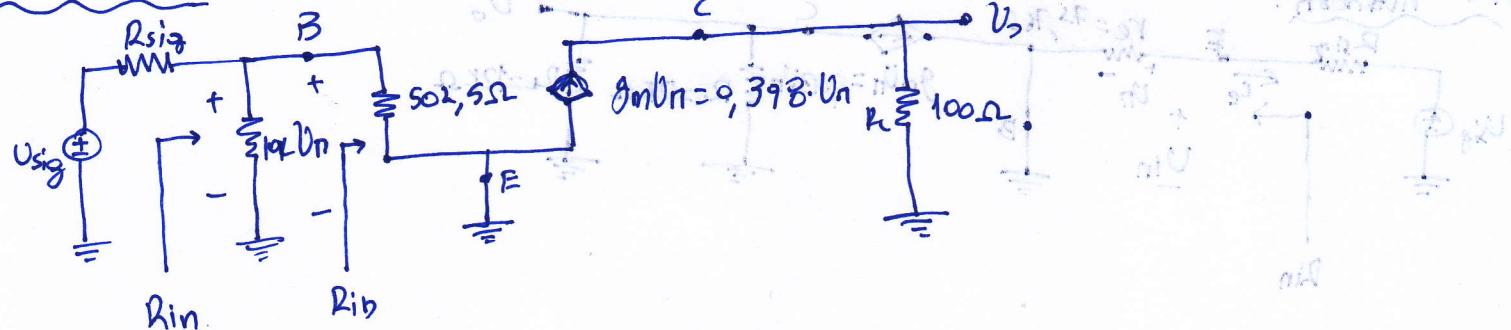

$$R_{in} = \frac{U_{in}}{I_{sig}} = \frac{10k \parallel 502,5}{10k \parallel 502,5 + R_{sig}} \cdot \frac{U_{sig}}{U_{sig}} = 10k \parallel 502,5 \Rightarrow R_{in} = 478,45\Omega = 0,478k\Omega$$

$$R_{ib} = \frac{U_n}{i_b} = \frac{r_D \cdot 10}{10} \Rightarrow R_{ib} = r_D = 502,5 \Omega$$

$$\frac{U_n}{U_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} = \frac{0,478}{0,478 + 1} = 0,323 \frac{V}{V}$$

$$\left\{ \begin{array}{l} \frac{U_o}{U_n} = -g_m R_C = -398,5 \cdot 100 \Omega = -39,85 \frac{V}{V} \\ \frac{U_o}{U_{sig}} = -39,85 \cdot 0,323 = -12,6 \frac{V}{V} \end{array} \right.$$

Av  $U_0 = 0,4V$  töre,


$$U_0 = 100 \cdot i_c = 100 \cdot g_m \cdot U_{IN} = 100 \cdot g_m \cdot i_b \cdot r_n = 100 \cdot g_m \cdot r_n \cdot \frac{10k}{10k+502,5} \cdot i_{sig} \Rightarrow$$

$$\Rightarrow U_0 = \frac{100 \cdot g_m \cdot r_n \cdot 10k}{10k+502,5} \cdot \frac{U_{sig}}{R_{sig} + 10k//502,5} \Rightarrow U_{sig} = \frac{(10 \cdot 502,5) \cdot (1,4785\Omega) \cdot 0,4V}{100 \Omega \cdot 502,5 \Omega \cdot 10k \Omega \cdot 0,398} \Rightarrow$$


$$\Rightarrow U_{sig} \approx \pm 0,03V$$

$$U_b = U_{sig} - i_{sig} \cdot R_{sig} = U_{sig} - \frac{U_{sig}}{1478,45} R_{sig} = \pm 0,13V$$

### Aufgabe 3

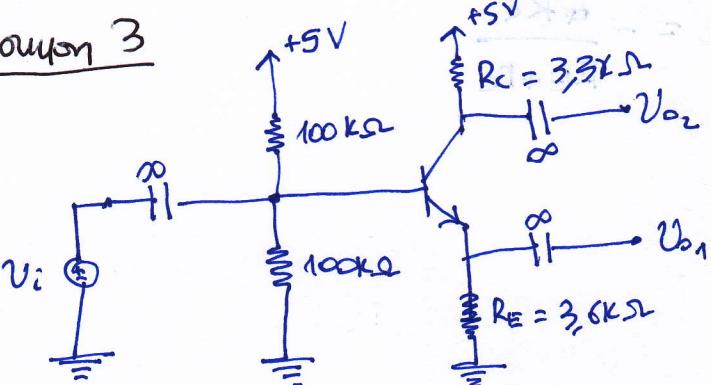

### DC Analysis:

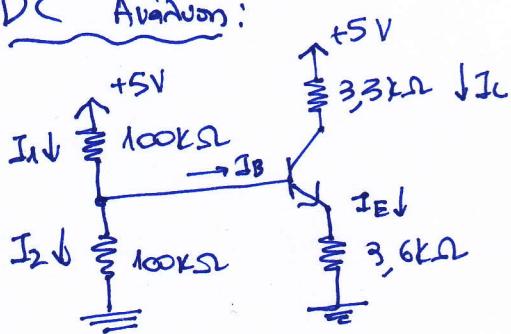

$$\beta = \infty : I_C = I_E, I_B = 0$$

$$NPK: I_1 = I_2 = I = \frac{5}{200k} = 0,025mA$$

$$NTK: 5 - I \cdot 100k = V_B \Rightarrow V_B = 5 - 2,5 \Rightarrow V_B = 2,5V$$

$$(V_{BE} \text{ ist } 0,7V)$$


$$\text{Ara } V_E = 1,8V$$

$$NTIC: V_F - I_E \cdot 3,6k = 0 \Rightarrow I_E = \frac{1,2V}{3,6k} \Rightarrow I_F = 0,33mA = I_C$$


$$g_m = \frac{I_C}{V_T} = 9,02$$

$$r_e = \frac{V_T}{I_C} = 50$$

### AC Analysis:

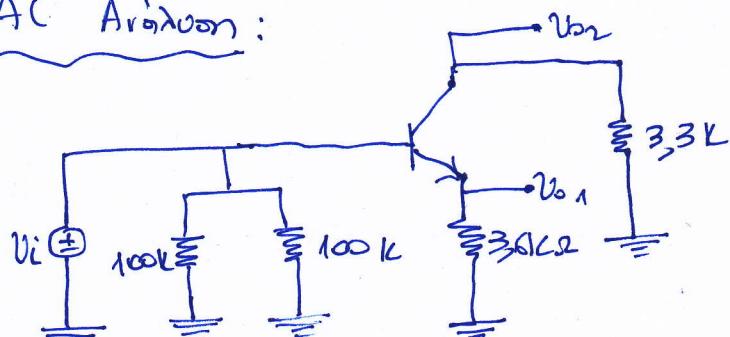

AVTILUDIMICROS TO BJT FOR PRACTICE :

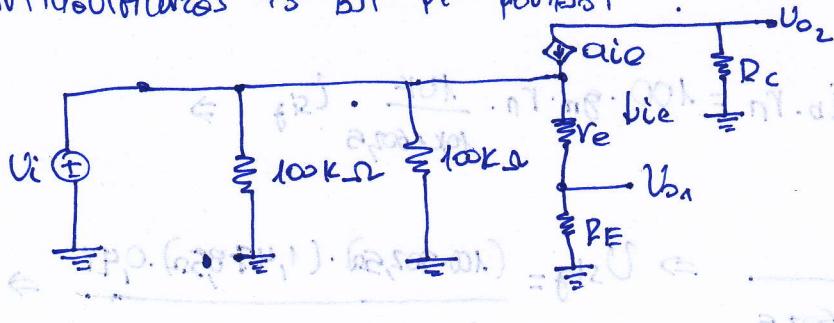

$$i_e = \frac{V_i}{R_E + r_e}$$

$$U_{o_1} = i_e R_E = V_i \cdot \frac{R_E}{R_E + r_e}$$

$$U_{o_2} = -a \cdot i_e R_C = -\frac{V_i}{R_E + r_e} \cdot R_C \Rightarrow \frac{U_{o_2}}{V_i} = -\frac{a R_C}{R_E + r_e}$$

$\Gamma_1 = a \approx 1$ :

$$r_e = \frac{V_T}{I_E} = \frac{25mV}{9.5mA} = 50\Omega$$

$$\frac{U_{o_1}}{V_i} = \frac{3,6}{3,6 + 0,05} = 0,986 \text{ V/V}$$


$$\frac{U_{o_2}}{V_i} = -\frac{3,3}{3,6 + 0,05} = 0,904 \text{ V/V}$$

$$\frac{U_{o_2}}{V_i} = -\frac{a R_C}{r_e} = -\frac{3,3}{0,05} = -66 \text{ V}$$

$$500 \cdot \frac{3,3}{50} = 0,66$$

$$0,66 \cdot \frac{V_i}{3,3} = 0,2 \text{ V}$$

## Acción 4

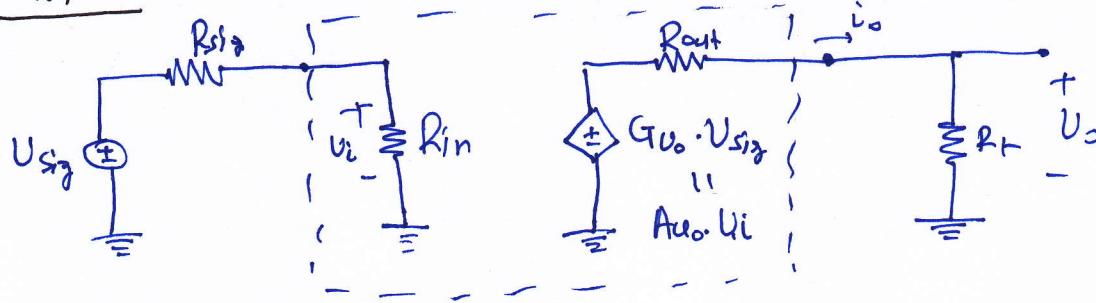

$$G_{U_0} = \frac{U_o}{U_{sig}} \Big|_{R_L=\infty}, \quad G_{U_0} = \frac{R_{in}}{R_{in} + R_{sig}} \Big|_{R_L=\infty}, \quad A_{U_0} = \frac{U_o}{U_i} \Big|_{R_i=\infty}, \quad R_i = \frac{R_{in}}{R_L} = \infty$$


$$R_L = \infty, \quad G_{U_0} = \frac{R_i}{R_i + R_{sig}} \Big|_{A_{U_0}}, \quad G_{T_u} = G_{U_0} \frac{R_L}{R_L + R_{out}}$$

Si  $R_L = \infty$ ,  $G_{U_0} = \frac{U_o}{U_i} \cdot \frac{U_i}{U_{sig}} = A_{U_0} \cdot \frac{U_i}{U_{sig}} = A_{U_0} \cdot \frac{U_{sig} \cdot R_i}{U_{sig}}$

$$G_{U_0} = \frac{R_i}{R_i + R_{sig}} \cdot A_{U_0}$$

Si  $R_L$  ncfp.,  $G_u = \frac{U_o}{U_{sig}} = \underbrace{\frac{R_L}{R_L + R_{out}}}_{\text{factores de carga}} \cdot G_{U_0} \cdot U_{sig} \cdot \frac{1}{U_{sig}} \Rightarrow G_u = \frac{R_L}{R_L + R_{out}} \cdot G_{U_0}$


## Acción 5

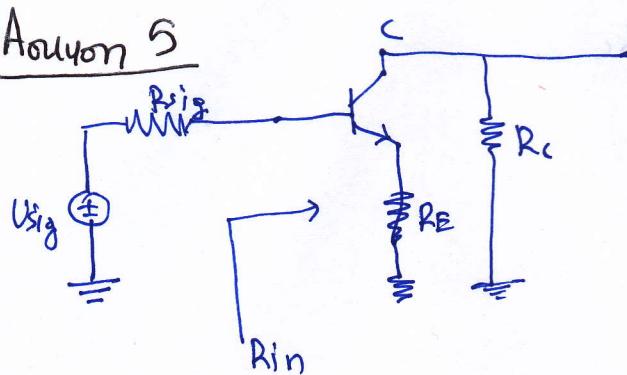

$$\beta = 74, \quad R_{in} = 15 k\Omega$$

$$\hat{U}_{sig} = 0.15V, \quad R_{sig} = 30 k\Omega \quad \hat{U}_{in} = 5mV$$

Movimiento T:

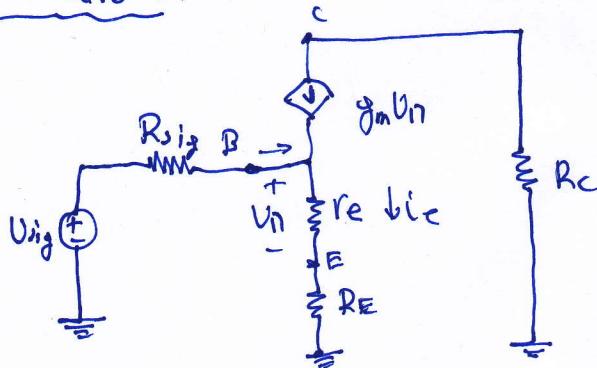


$$R_{in} = (\beta + 1)(r_e + R_E)$$

$$R_E + r_e = \frac{R_{in}}{\beta + 1}$$

$$U_{in} = \frac{r_e}{R_{sig} + R_E + r_e} U_{sig} \Rightarrow U_{in} (R_{sig} + R_E + r_e) = U_{sig} \cdot r_e$$

$$r_e = \frac{B}{B+1} \cdot \frac{V_T}{I_C} \Rightarrow I_C = \frac{BV_T}{(B+1) \cdot R_E}$$

Aufgabe 6

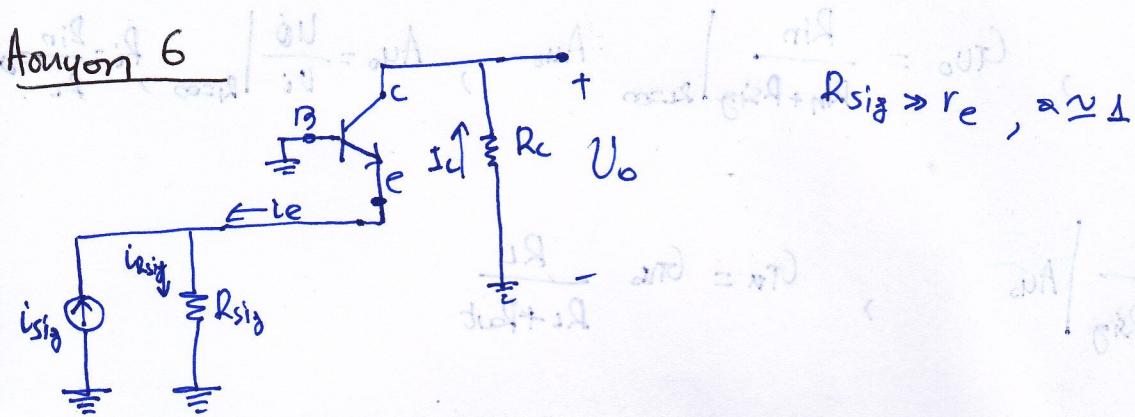

$$\alpha \approx 1 \Rightarrow U_C \approx i_e$$

$$NTK: V_{BE} = i_{R_{sig}} \cdot R_{sig} \Rightarrow i_{R_{sig}} = \frac{V_{BE}}{R_{sig}}$$

$$i_e = i_{R_{sig}} - i_{sig} \Rightarrow i_e = i_c = \frac{V_{BE}}{R_{sig}} - i_{sig}$$

$$U_o = -i_c \cdot R_C \Rightarrow U_o = \left( i_{sig} - \frac{V_{BE}}{R_{sig}} \right) R_C$$




$$(1 + \beta) (1 + \beta) = 100$$


$$\beta = \frac{\beta_1}{\beta_2}$$

$$100 = (1 + \beta_1) (1 + \beta_2) \approx \beta_1 \cdot \beta_2 \Rightarrow \frac{\beta_1 \cdot \beta_2}{\beta_1 + \beta_2} = 100$$
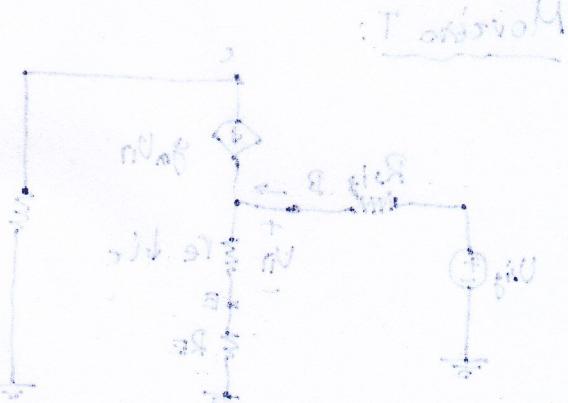
$$= \frac{\beta_1 \cdot \beta_2}{\beta_1 + \beta_2} = 1 \Leftrightarrow \frac{\beta_1}{\beta_1 + \beta_2} = 99$$



# Aufgabe 7

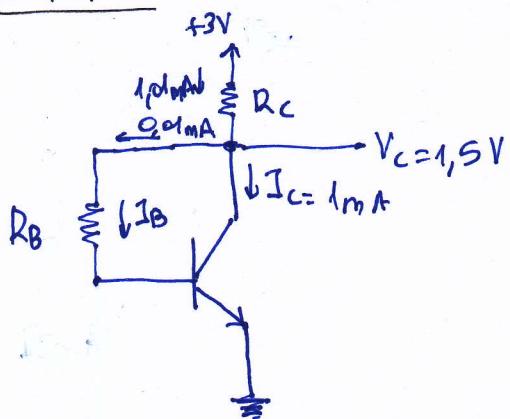

$$a) R_C = \frac{3 - 1,5}{1,61 \text{ mA}} \approx 1,5 \text{ k}\Omega$$


$$1,5 = 0,01 R_B + V_{BE} = 0,01 R_B + 0,7 \Rightarrow R_B = 80 \text{ k}\Omega$$

b) 5%:  $R_C = 1,5 \text{ k}\Omega, R_B = 82 \text{ k}\Omega$

$$I_E = \frac{V_{CC} - V_{BE}}{R_C + \frac{R_B}{\beta+1}} = \frac{3 - 0,7}{1,5 + \frac{82}{101}} = 0,999 \text{ mA}$$

$$I_C = \alpha I_E = 0,999 \times 0,999 = 0,99 \text{ mA}$$
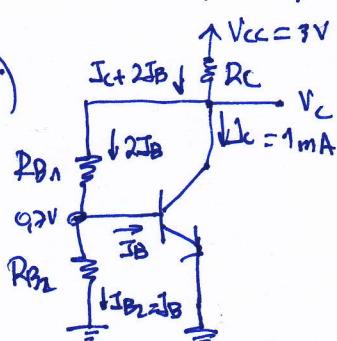
$$V_C = 3 - 1,5 \times 0,99 = 1,52 \text{ V}$$



$$I_B = \frac{I_C}{\beta} = \frac{1}{100} = 0,01 \text{ mA}$$

$$R_{B2} = \frac{97}{I_{B2}} = \frac{97}{0,01} = 9700 \text{ }\Omega$$

$$1,5 = 2I_B \cdot R_{B1} + 0,7 \Rightarrow 0,8 = 2 \cdot 0,01 \cdot R_{B1} \Rightarrow R_{B1} = 40 \text{ k}\Omega$$

$$R_C = \frac{3 - 1,5}{I_C + 2I_B} = \frac{1,5}{1,02} = 1,47 \text{ k}\Omega$$

f)  $\beta = \infty$ :

$$I_B = 0, I_{B2} = \frac{0,7}{R_{B2}} = \frac{0,7}{70} = 0,01 \text{ mA}$$


$$I_{B1} = I_{B2} = 0,01 \text{ mA}$$

$$V_C = 0,01 R_{B1} + 0,7 = 0,01 \cdot 40 + 0,7 = 1,1 \text{ V}$$

$$I_C + 901 = \frac{3 - 1,1}{R_C} = \frac{3 - 1,1}{1,47} = 1,29 \Rightarrow I_C = 1,28 \text{ mA}$$



# Aufgabe 8

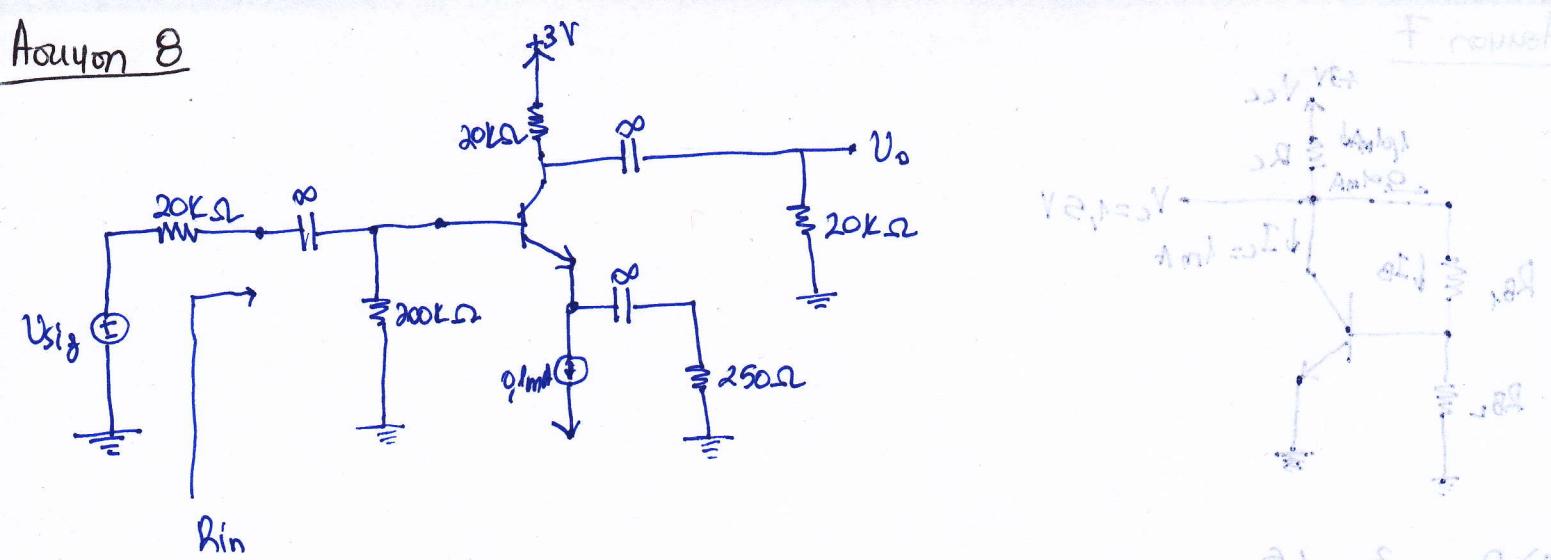

$$I_E = 0,1 \text{ mA}$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{0,1 \text{ mA}} = 250 \Omega$$

$$g_m = \frac{I_C}{V_T} \approx \frac{0,1 \text{ mA}}{0,025 \text{ V}} = 4 \text{ mA/V}$$

$$R_E = 250 \Omega$$

$$R_{in} = 200 \Omega \parallel (\beta + 1)(r_e + R_E) = 200 \parallel [101 \times (0,25 + 0,25)] = 200 \parallel 50,5 = 40,3 \text{ k}\Omega$$

$$\frac{V_b}{V_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} = \frac{40,3}{40,3 + 20} \approx 0,668 \text{ V/V}$$

$$\frac{V_o}{V_b} = -\beta \frac{\text{Output-Aussteuerung}}{\text{Input-Aussteuerung}} \approx -\frac{20 \parallel 20}{0,25 + 0,25} = -20 \text{ V/V}$$


$$G_{rv} = \frac{V_o}{U_{sig}} = \frac{V_o}{V_b} \cdot \frac{V_b}{V_{sig}} = -0,668 \times 20 = -13,4 \text{ V/V}$$

Für  $V_{be}$  relop. zu 5mV, so mit Kond. passen nur geringe Differenz von 10mV.


$$\hat{V}_{sig} = \frac{10 \text{ mV}}{\frac{V_b}{U_{sig}}} = \frac{10 \text{ mV}}{0,668 \text{ V/V}} = 15 \text{ mV}$$

$$\text{Daher, } V_o = |G_{rv}| \cdot \hat{V}_{sig} = 13,4 \times 15 = 200 \text{ mV} = 0,2 \text{ V}$$

### Aufgabe 9

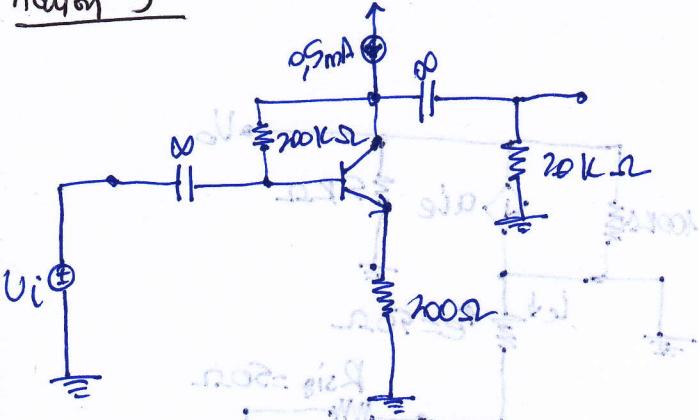


a)

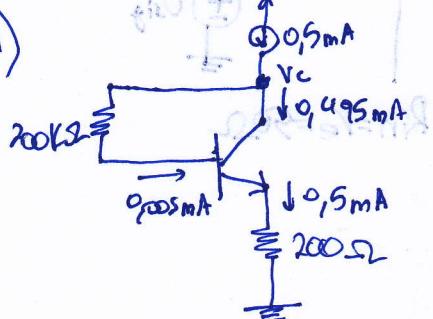

$$I_C = 0,495 \text{ mA}$$

$$\begin{aligned} V_C &= I_B \times 200\text{k}\Omega + I_E \times 0,2\text{k}\Omega + V_{BE} \\ &= 0,005 \times 200 + 0,5 \times 0,2 + 0,7 \\ &= 1,18 \text{ V} \end{aligned}$$

b)

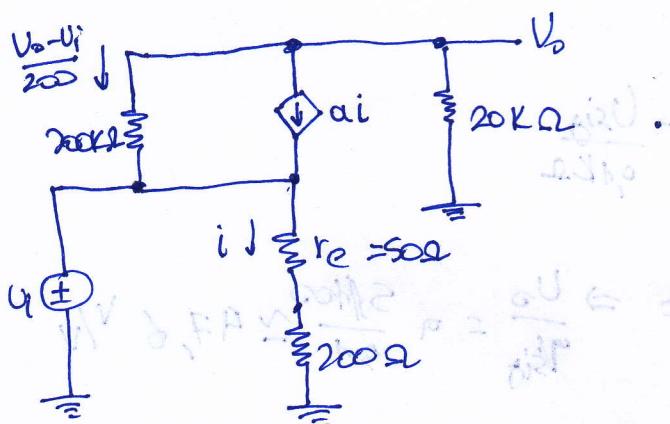

$$g_m = \frac{I_C}{V_T} = \frac{0,495}{0,025} \approx 20 \text{ mA/V}$$

$$r_e = \frac{V_T}{I_E} = 50 \Omega$$

$$i = \frac{V_i}{r_{e+R_L}} = \frac{V_i}{50 + 200} = \frac{V_i}{250} = 4V_i \text{ (mA)}$$



$$\frac{U_o}{20} + ai + \frac{U_o - U_i}{200} = 0 \Rightarrow$$

$$\Rightarrow \frac{U_o}{20} + 0,99 \times 4V_i + \frac{U_o}{200} - \frac{U_i}{200} = 0$$

$$\Rightarrow U_o \left( \frac{1}{20} + \frac{1}{200} \right) = -U_i \left( 4 \cdot 0,99 - \frac{1}{200} \right)$$

$$\Rightarrow \frac{U_o}{U_i} = -7,9 \text{ V/mm}$$

## Aufgabe 10

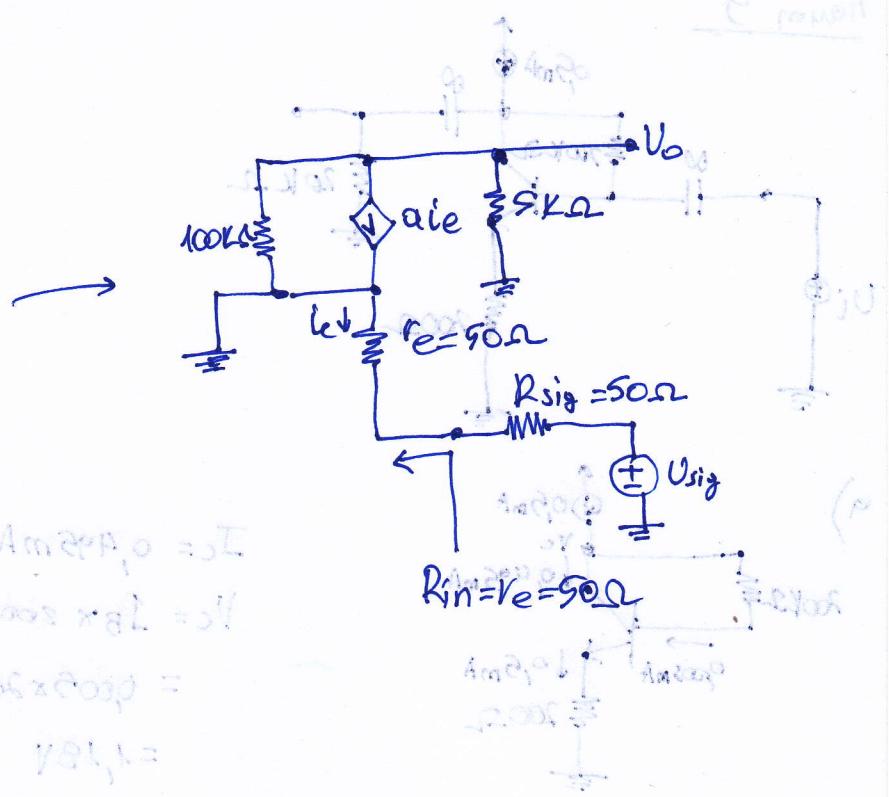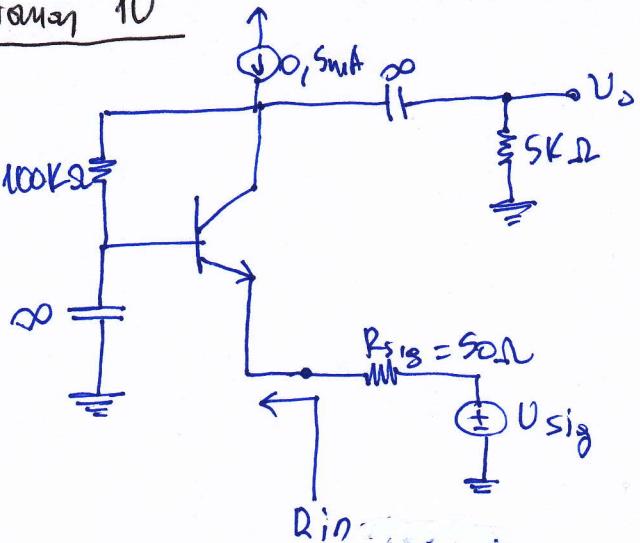

$$I_C = \alpha I_E \approx 0.5 \text{ mA}$$

$$R_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{0.5 \text{ mA}} = 50\Omega$$


$$R_{in} = R_e = 50\Omega$$

$$i_e = -\frac{U_{sig}}{R_e + R_{sig}} = -\frac{U_{sig}}{50 + 50} = -\frac{U_{sig}}{100} = -\frac{U_{sig}}{0.1k\Omega}$$


$$U_o = -\alpha \cdot i_e \cdot (5/100) = \alpha \frac{U_{sig}}{100} \cdot (5/100)$$

$$\Rightarrow \frac{U_o}{U_{sig}} = \alpha \frac{5/100}{0.1} \approx 47,6 \text{ V/V}$$

## Aufgabe 11

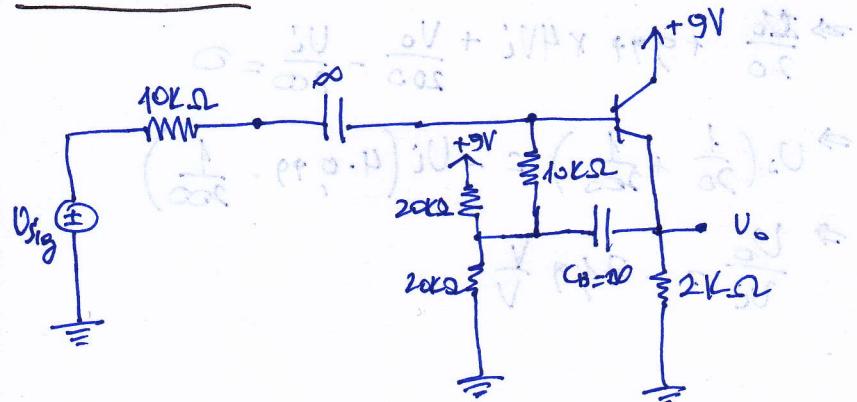

DC 1005. (p + Thevenin):

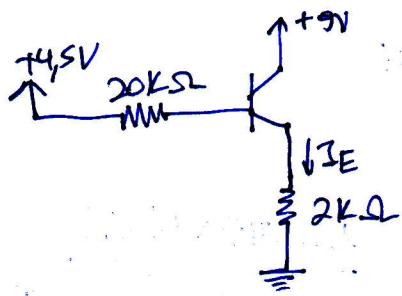

$$a) I_E = \frac{4,5 - 0,7}{2 + \frac{20}{\beta+1}} = \frac{3,8}{2 + \frac{20}{101}} = 1,73 \text{ mA}$$


$$I_C = \alpha I_E = 0,99 \times 1,73 \text{ mA} = 1,71 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = 68,4 \text{ mA/V}$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{1,73 \text{ mA}} = 14,5 \Omega = 0,0145 \text{ k}\Omega$$

$$r_h = (\beta + 1)r_e = 101 \times 0,0145 = 1,4645 \text{ k}\Omega$$

b) Longo "T" ( $r_o = \infty$ )

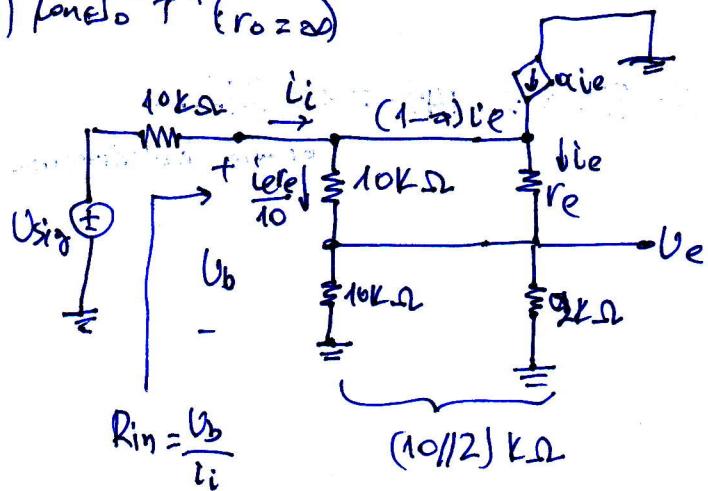

$$V_e = (i_e + i_e \frac{r_e}{10}) (10/2)$$

$$V_b = V_c + i_e r_e = i_e (10/2) \cdot (1 + \frac{r_e}{10}) + i_e r_e$$


$$i_i = (1 - \alpha) i_e + i_e \frac{r_e}{10} = \frac{i_e}{\beta+1} + i_e \frac{r_e}{10}$$

$$\begin{aligned} R_{in} &= \frac{V_b}{i_i} = \frac{(10/2) \cdot (1 + \frac{r_e}{10}) + r_e}{\frac{1}{\beta+1} + \frac{r_e}{10}} = \frac{(\beta+1)(10/2)(1 + \frac{r_e}{10}) + (\beta+1)r_e}{(\beta+1)\frac{r_e}{10} + 1} = \\ &= \frac{101 \times (10/2) \times (1 + 0,00145) + 101 \times 0,00145}{1 + 101 \times 0,00145} = 148,3 \text{ k}\Omega \end{aligned}$$

$$\frac{U_b}{U_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} = \frac{148,3}{148,3 + 10} = 0,937$$

$$\frac{U_o}{U_b} = \frac{U_e}{U_b} = \frac{i_e \left(1 + \frac{r_e}{10}\right) (10/2)}{i_e \left(1 + \frac{r_e}{10}\right) (10/2) + i_e r_e} = \frac{1,00145 \times (10/2)}{1,00145 \times (10/2) + 0,0145} = 0,991 \text{ V/V}$$
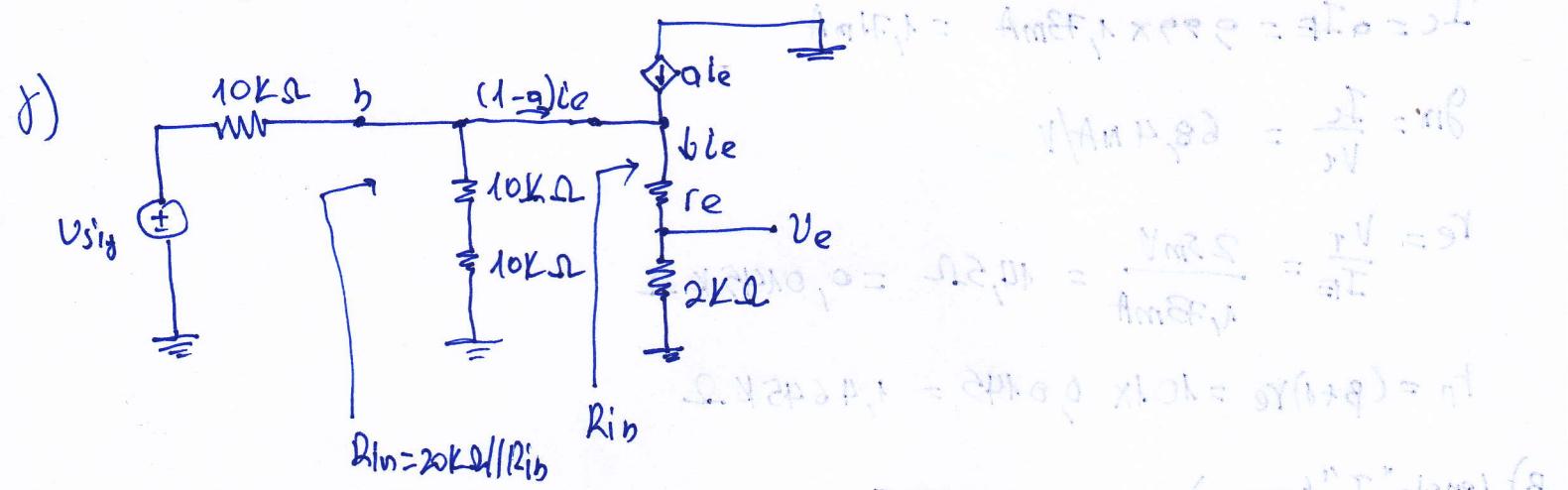
$$G_V = \frac{U_o}{U_{sig}} = 0,937 \times 0,991 = 0,93 \text{ V/V}$$



$$R_{in} = 20\text{k}\Omega / R_{ib} = 20\text{k}\Omega / (\beta + 1)(R_{et} + 2) = 20 / (101 \times 3,0145) = 18,21\text{k}\Omega$$

$$\frac{U_b}{U_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} = \frac{18,21}{28,21} = 0,646 \text{ V/V}$$


$$\frac{U_o}{U_b} = \frac{2}{2 + 0,0145} = 0,993$$

$$G_V = \frac{U_o}{U_{sig}} = 0,646 \times 0,993 = 0,64 \text{ V/V}$$


$$= \frac{2(1+g) + \left(\frac{2}{2+g} + 1\right)(2+g)(1+g)}{1 + \frac{2}{2+g}(1+g)}$$

$$R_{in} = 20\text{k}\Omega / R_{ib} + (2+0,0145) \times (2+0,0145) \times 100 =$$

## Aufgabe 12

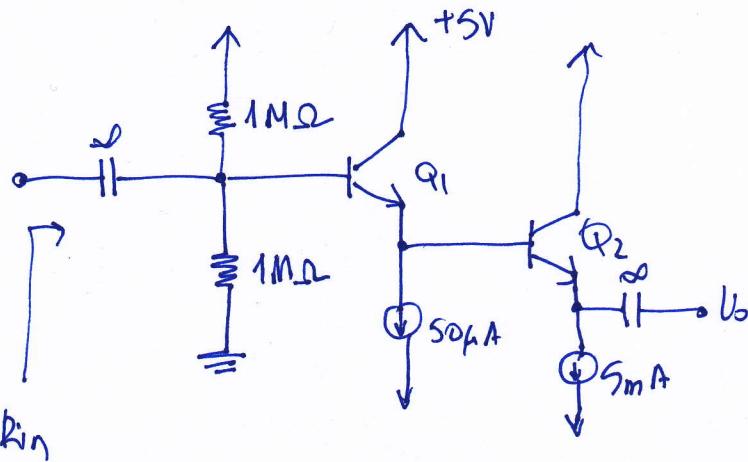

a) DC (if Thevenin):

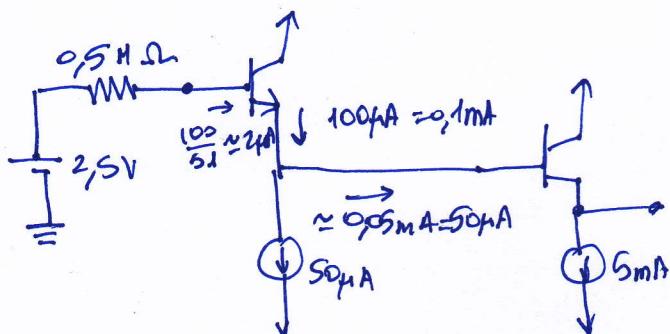

$$I_{E1} = 0,1 \text{ mA}$$

$$I_{E2} = 5 \text{ mA}$$

$$V_{B1} = 2,5 - 2 \cdot 4 \text{ k} \Omega \cdot 0,1 \text{ mA} = 1,5 \text{ V}$$

$$V_{B2} = V_{B1} - 9,7 = 9,8 \text{ V}$$

b)  $R_L = 1 \text{ k} \Omega$

$$\frac{U_o}{U_{B2}} = \frac{R_L}{R_L + r_{e2}}$$

$$r_{e2} = \frac{25 \text{ mV}}{5 \text{ mA}} = 5 \text{ } \Omega$$

$$\frac{U_o}{U_{B2}} = \frac{1000}{1000 + 5} = 0,995 \text{ V/V}$$

$$R_{iB2} = (\beta_2 + 1)(r_{e2} + R_L) = 101 \times 1,005 = 101,5 \text{ k} \Omega$$

$$\delta) R_{in} = 1 \text{ M} \Omega // 1 \text{ M} \Omega // (\beta + 1)(r_{e1} + R_{iB2})$$

$$r_{e1} = \frac{V_T}{I_{E1}} = \frac{25 \text{ mV}}{0,1 \text{ mA}} = 250 \text{ } \Omega = 0,25 \text{ k} \Omega$$

$$R_{in} = 0,5 \text{ M} \Omega // [51 \times (0,25 + 101,5)] \text{ k} \Omega = 0,5 \text{ M} \Omega // 5,2 \text{ M} \Omega = 450 \text{ k} \Omega$$

$$\frac{U_{re1}}{U_{B1}} = \frac{R_{iB}}{R_{iB} + r_{e1}} = \frac{101,5}{101,5 + 0,25} = 0,9975 \text{ V/V}$$

$$\delta) \frac{U_{B1}}{U_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} = \frac{450}{450 + 100} = 0,82 \text{ V/V}, \quad \delta) \frac{U_o}{U_{sig}} = 0,82 \times 0,9975 \times 0,995 = 0,814 \text{ V} \quad 13$$